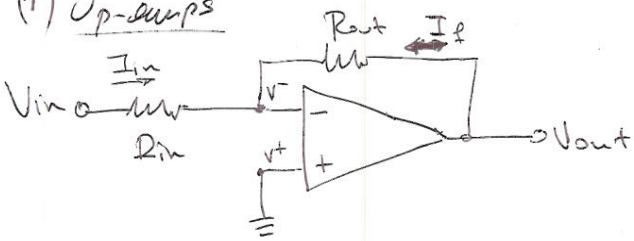


MAS. 862 P. I. T.

Chapter 14 Problem Set

(1) Op-amps



$$I_{in} = -\frac{V^- - V_{in}}{R_{in}}$$


$$I_f = \frac{V_{out} - V^-}{R_{out}}$$

$$V^- = V^+ = 0$$

$$I_{in} = -I_f$$

$$\Rightarrow -\frac{V_{in}}{R_{in}} = \frac{V_{out}}{R_{out}}$$
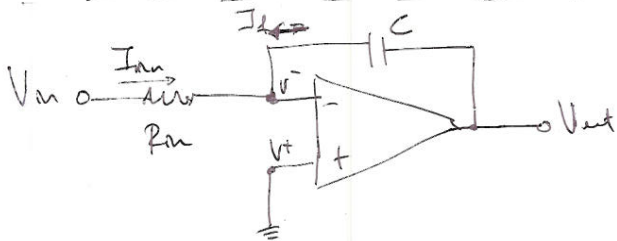
$$\Rightarrow V_{out} = -\frac{R_{out}}{R_{in}} V_{in}$$



$$I_{in} = -\frac{V^- - V_{in}}{R_{in}}$$


$$I_f = C \frac{d(V_{out} - V^-)}{dt}$$

$$V^- = V^+ = 0$$

$$I_{in} = -I_f$$

$$\Rightarrow -\frac{V_{in}}{R_{in}} = C \frac{dV_{out}}{dt}$$
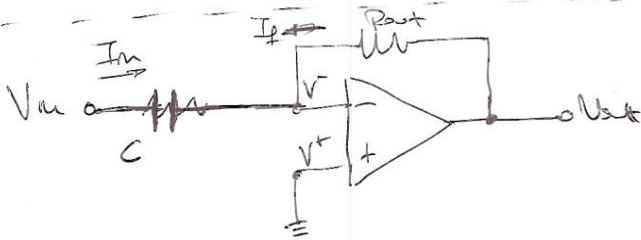
$$\Rightarrow V_{out} = -\frac{1}{R_{in} C} \int V_{in} dt$$



$$I_{in} = C \frac{d(V^- - V_{in})}{dt}$$


$$I_f = \frac{V_{out} - V^-}{R_{out}}$$

$$V^- = V^+ = 0$$

$$I_f = -I_{in}$$

$$\Rightarrow -C \frac{dV_{in}}{dt} = \frac{V_{out}}{R_{out}}$$
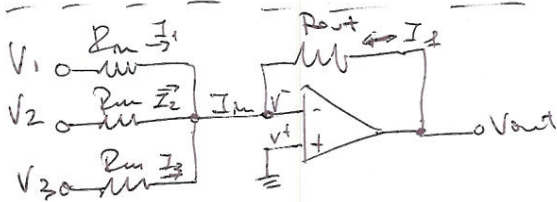
$$\Rightarrow V_{out} = -R_{out} C \frac{dV_{in}}{dt}$$




$$I_{in} = I_1 + I_2 + I_3 = -\frac{V^- - (V_1 + V_2 + V_3)}{R_{in}}$$

$$I_f = \frac{V_{out} - V^-}{R_{out}}$$

$$V^- = V^+ = 0$$

$$I_f = -I_{in}$$
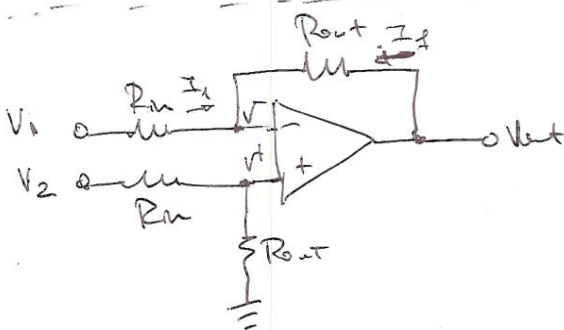
$$\Rightarrow V_{out} = -\frac{R_{out}}{R_{in}} (V_1 + V_2 + V_3)$$



$$I_1 = -\frac{V^- - V_1}{R_{in1}} \quad (1)$$

$$I_f = \frac{V_{out} - V^-}{R_{out}} \quad (2)$$

$$(3) \quad V^- = V^+ = \frac{R_{out}}{R_{in1} + R_{out}} \cdot V_2$$


$$(4) \quad I_1 = -I_f$$

$$\Rightarrow R_{out}(V^- - V_1) = R_{in1}(V_{out} - V^-)$$

$$\Rightarrow (R_{in1} + R_{out})V^- = R_{in1}V_{out} + R_{out}V_{in}$$

$$\Rightarrow R_{out}V_2 = R_{in1}V_{out} + R_{out}V_{in}$$

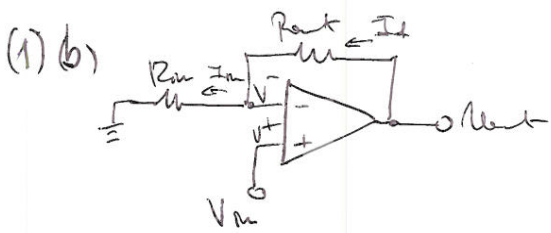
$$\Rightarrow V_{out} = \frac{R_{out}}{R_{in1}} (V_2 - V_{in})$$




$$\begin{aligned}
 I_{in} &= \frac{V^- - 0}{R_{in}} \\
 I_f &= \frac{V_{out} - V^-}{R_{out}} \\
 V^- &= V^+ = V_{in} \\
 I_f &= I_{in}
 \end{aligned}
 \left. \begin{aligned}
 &\Rightarrow \frac{V_{in}}{R_{in}} = \frac{V_{out} - V_{in}}{R_{out}} \\
 &\Rightarrow V_{out} = R_{out} \cdot \left(\frac{1}{R_{in}} + \frac{1}{R_{out}} \right) V_{in} \\
 &\Rightarrow \boxed{V_{out} = \left(1 + \frac{R_{out}}{R_{in}} \right) V_{in}}
 \end{aligned} \right\}$$

Reasons not used

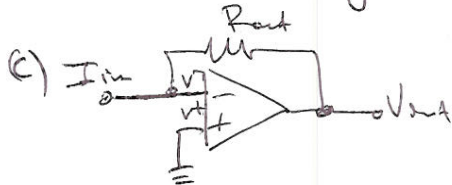
- $Gain > 1$ always
- Cannot sum voltages without common-mode rejection (voltages vs current sum)


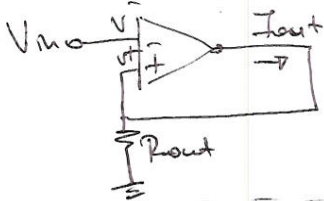
$$\begin{aligned}
 -\frac{V_{out} + V^-}{R_{out}} &= I_{in} \\
 V^- &= V^+ = 0
 \end{aligned}
 \left. \right\} \Rightarrow \boxed{V_{out} = -R_{out} I_{in}}$$


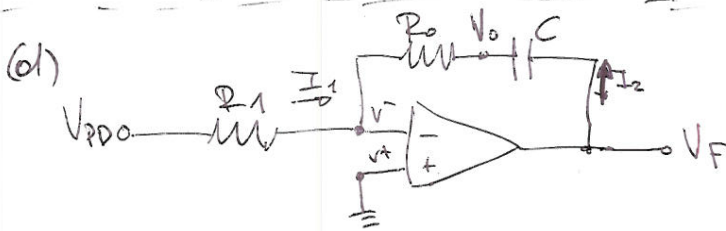
$$\begin{aligned}
 V^+ &= I_{out} \cdot R_{out} \\
 V^- &= V^+ = V_{in}
 \end{aligned}
 \left. \right\} \Rightarrow \boxed{I_{out} = \frac{V_{in}}{R_{out}}}$$



$$\begin{aligned}
 \frac{-V^- + V_{DD0}}{R_1} &= I_1 \quad \text{①} & V^- &= V^+ = 0 \quad \text{④} \\
 \frac{V_0 - V^-}{R_0} &= I_2 \quad \text{②} & I_1 &= -I_2 \quad \text{⑤} \\
 C \frac{d(V_F - V_0)}{dt} &= I_2 \quad \text{③}
 \end{aligned}$$

So we have


$$\left. \begin{aligned}
 \text{①, ③, ⑤} &: \frac{V_{DD0}}{R_1} = C \frac{d(V_F - V_0)}{dt} \Rightarrow \frac{V_{DD0}}{R_1} = C \frac{dV_F}{dt} + C \frac{dV_0}{dt} \\
 \text{①, ②, ⑤} &: \frac{V_{DD0}}{R_1} = -\frac{V_0}{R_0} \Rightarrow V_0 = -V_{DD0} \cdot \frac{R_0}{R_1}
 \end{aligned} \right\} \Rightarrow$$

$$\Rightarrow \frac{V_{DD0}}{R_1} = -C \frac{dV_F}{dt} - C \frac{R_0}{R_1} \frac{dV_{DD0}}{dt}$$

$$\Rightarrow \boxed{\frac{dV_F}{dt} = -\frac{R_0}{R_1} \frac{dV_{DD0}}{dt} - \frac{V_{DD0}}{R_1 C}}$$

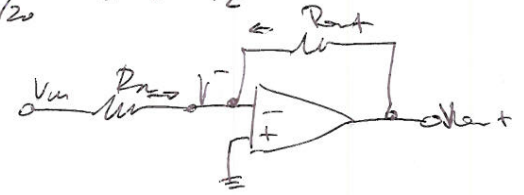(14.2) We have eq (14.3) $\Rightarrow \omega_{ol} = \frac{\omega_{cl}}{G_{ol}} = \frac{10^6 \text{ Hz}}{10^{100/20}} = 10 \text{ Hz}$

For the ~~non~~-inverting amplifier we have



By definition $G_{ol} = -\frac{V_{out}}{V^-}$ (op-amp)

and we have $\frac{V_{in} - V^-}{R_{in}} = -\frac{V_{out} - V^-}{R_{out}} \Rightarrow V^- = \left(\frac{V_{in} + V_{out}}{\frac{R_{in}}{R_{out}} + 1} \right) \cdot \frac{R_{in} + R_{out}}{R_{in} \cdot R_{out}}$

Substituting $-\frac{V_{out}}{G_{ol}} = \left(\frac{V_{in} + V_{out}}{\frac{R_{in}}{R_{out}} + 1} \right) \cdot \frac{R_{in} + R_{out}}{R_{in} \cdot R_{out}} = \frac{(R_{out}/V_{in} + R_{in} V_{out}) (R_{in} + R_{out})}{(R_{in} \cdot R_{out})^2}$

$\Rightarrow \frac{V_{out}}{V_{in}} = -\frac{G_{ol} R_{out}/R_{in}}{G_{ol} + 1 + R_{out}/R_{in}} = \frac{G_{ol}}{1 + \frac{R_{out}}{R_{in}} + \frac{R_{in}}{G_{ol} R_{in}}}$

Using (14.2) we have $G_{ol}(\omega) = \frac{G_{ol}}{1 + i \frac{\omega}{\omega_{ol}}} = \frac{G_{ol}}{1 + i \omega_{ol}}$

(14.3) $f_{osc} = 100 \text{ kHz}$

$Q_{BPF} = 50$ no filter width: 2 kHz

$\tau_{LPF} = 1 \text{ s} \Rightarrow f_{LPF} = 1 \text{ Hz}$

$f_{imp,max} = 1 \text{ MHz}$


$\frac{SNR_{out}}{SNR_{in}} = \frac{S^2/B}{P_{in}/B_0} \cdot \frac{P_{in} B_0}{S^2/B} = \frac{B_1}{B_0}$

noise is AWGN

from the BPF: $10 \log \frac{10^3}{10^6} = -33 \text{ dB}$

from the LPF: $10 \log \frac{10^1}{2 \cdot 10^3} = -20 \text{ dB}$

Assuming SNR 10dB

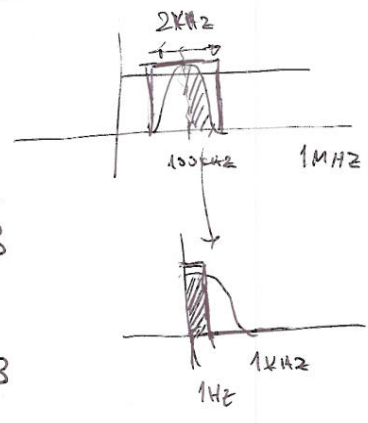

(14.4) ^(a) we have $X_n = X_{n-1} + X_{n-4} \pmod{2}$

Thus:

X_{n-4}	X_{n-3}	X_{n-2}	X_{n-1}	X_n
1	1	1	1	0
1	1	1	0	1
1	1	0	1	0
1	0	1	0	1
0	1	0	1	1
1	0	1	1	0
0	1	1	0	0
1	1	0	0	1
1	0	0	1	0
0	0	1	0	0

etc

(b) Age of universe ≈ 10 billion years $= 10^{10}$ years $\approx 10^{17}$ seconds
 Assuming one cycle per nanosecond, we have
 chip rate $(2^n - 1) \times 10^{-9} \text{ s} = 10^{17} \text{ s} \Rightarrow n \approx 86$

(c) $CG = 10 \log_{10} \frac{SNR_{FSK}}{SNR_{BPSK}} = 10 \log_{10} \frac{2^{26}}{1} \approx 260 \text{ dB}$

(14.5) $SNR_{\text{dB, bit}} = 20 \log_{10} 2^8 \approx 48 \text{ dB}$

$SNR_{\text{dB, 16 bit}} = 20 \log_{10} 2^{16} \approx 96 \text{ dB}$

(14.6) Received: 0010 0111 00

The Trellis diagram for 5 states looks like this

