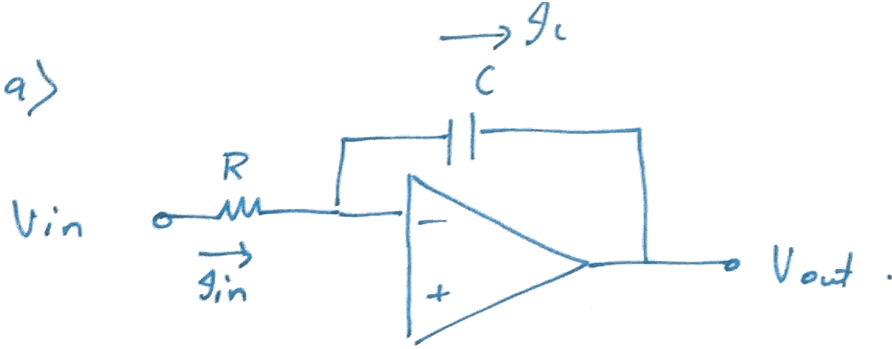


14.1 a)



$$I_{in} = \frac{V_{in}}{R}$$

All the current goes through C.


$$I_{in} = I_c = \frac{V_{out}}{X_c} = \frac{V_{in}}{R}$$

$$I_c = C \frac{dV_c}{dt} = C \left(-\frac{dV_o}{dt} \right)$$

$$-C \frac{dV_o}{dt} = \frac{V_{in}}{R}$$

$$\frac{dV_o}{dt} = \frac{-1}{Rc} V_{in}$$


$$V_o = \frac{-1}{Rc} \int V_{in} dt$$

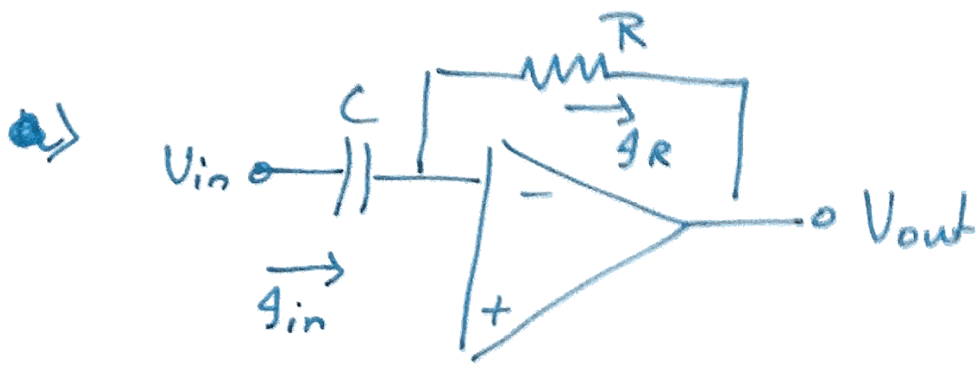

$$I_{in} = I_R$$

$$C \frac{dV_c}{dt} = \frac{-V_{out}}{R} \Rightarrow C \frac{dV_{in}}{dt} = \frac{-V_{out}}{R}$$


$$V_{out} = -RC \frac{dV_{in}}{dt}$$

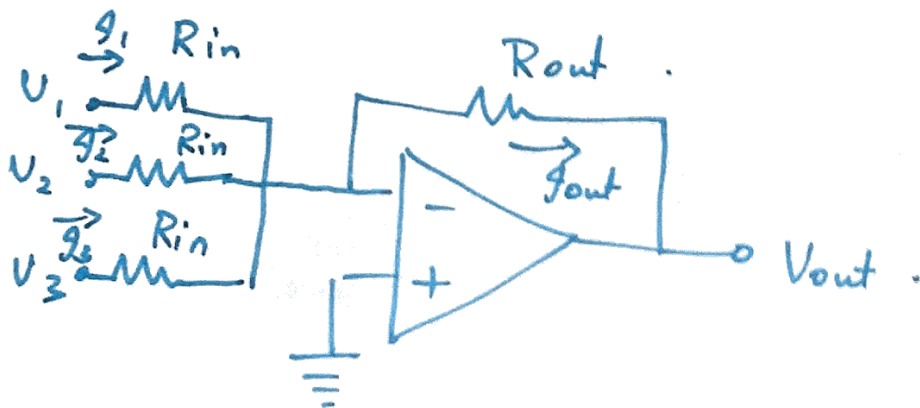

$$I_{out} = I_1 + I_2 + I_3 \quad (\text{Assuming virtual ground})$$

$$\frac{-V_{out}}{R_{out}} = \frac{V_1}{R_{in}} + \frac{V_2}{R_{in}} + \frac{V_3}{R_{in}}$$
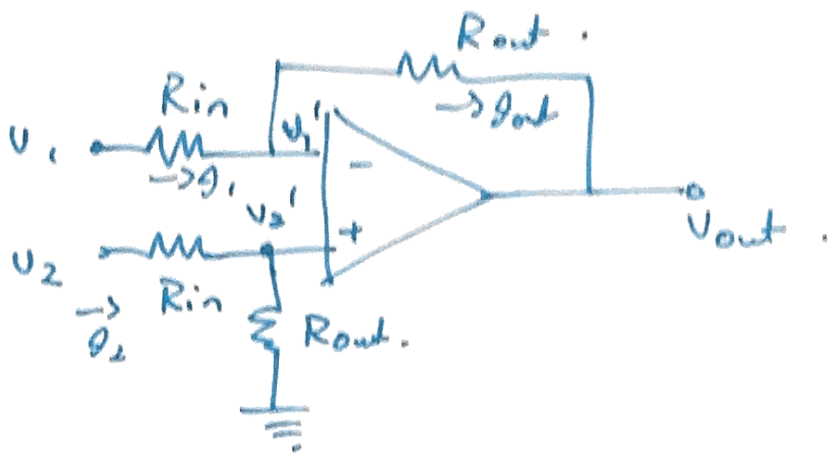
$$V_{out} = -\frac{R_{out}}{R_{in}} (V_1 + V_2 + V_3)$$



When $V_2 = 0$, $I_1 = I_{out}$

$$V_{out1} = \frac{-R_{out}}{R_{in}} V_1$$

When $V_1 = 0$, $V_2' = \frac{R_{out}}{R_{in} + R_{out}} V_2$.

$$V_1' = V_2' \quad \text{and} \quad I_1 = \frac{V_1 - V_1'}{R_{in}} = \frac{-V_1'}{R_{in}} = \frac{-V_2'}{R_{in}}$$


$$I_1 = \frac{-V_2'}{R_{in}} \left(\frac{R_{out}}{R_{in} + R_{out}} \right) = I_{out} = \frac{V_1' - V_{out}''}{R_{out}}$$

$$= \frac{\frac{R_{out}}{R_{in} + R_{out}} V_2 - V_{out}''}{R_{out}} = \frac{V_2}{R_{in} + R_{out}} - \frac{V_{out}''}{R_{out}}$$

$$V_{out} = V_{out1} + V_{out2} = \frac{-R_{out}}{R_{in}} V_1 + \frac{R_{out}}{R_{in}} V_2$$


$$\underline{\underline{V_{out} = \frac{R_{out}}{R_{in}} (V_2 - V_1)}}$$

14.9 (b)

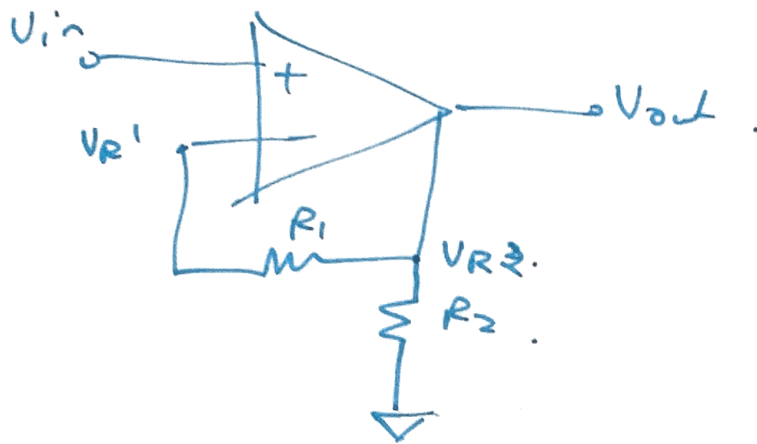

$$V_{R2} = V_{out} = V_{R1} \frac{R_2}{(R_1 + R_2)} = V_{in} \frac{R_2}{(R_1 + R_2)}$$

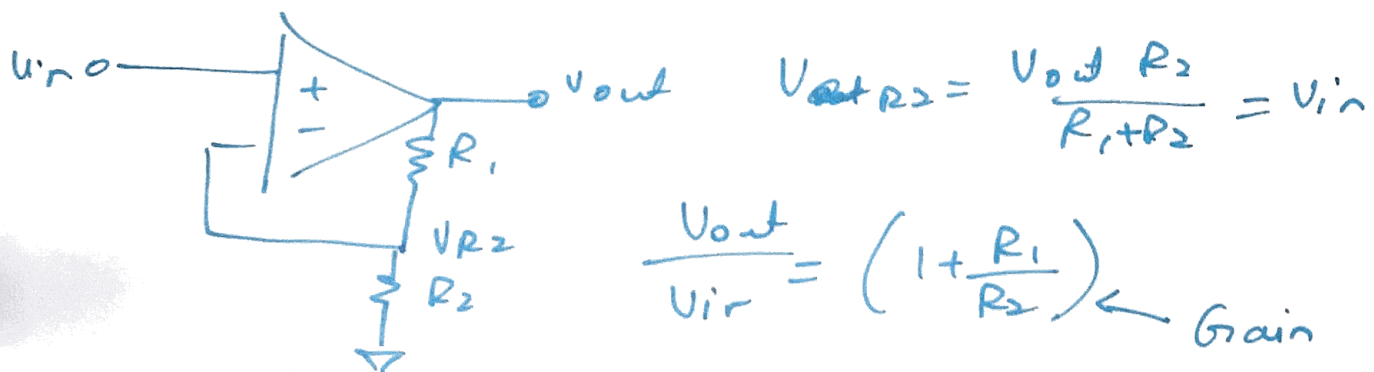
$$\frac{V_{out}}{V_{in}} = \frac{R_2}{(R_1 + R_2)} \quad (\text{Not an amplifier})$$




$$V_{out} R_2 = V_{in} \frac{R_2}{R_1 + R_2} = V_{in}$$

$$\frac{V_{out}}{V_{in}} = \left(1 + \frac{R_1}{R_2}\right) \leftarrow \text{Gain}$$

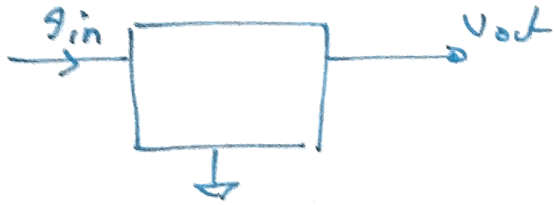(c) Gain for a transimpedance amplifier =




$$V_{out} \propto g_{in}$$

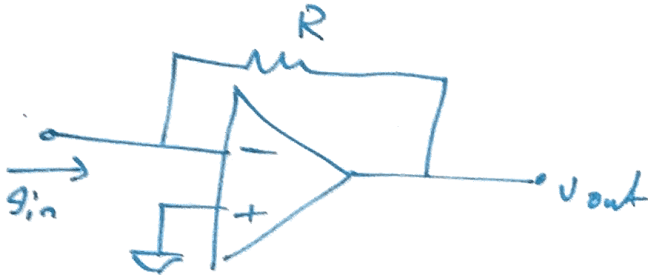

$$\frac{-V_{out}}{R} = g_{in}$$

$$V_{out} = -g_{in} R$$

Trans conductance amplifiers

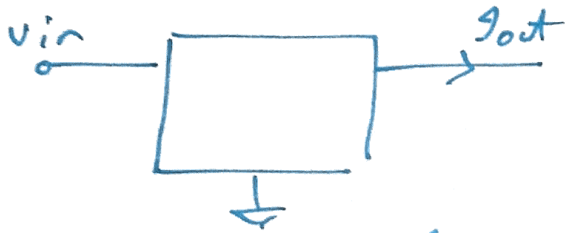


$$g_{out} \propto V_{in}$$



$$g_{in} = g_{R_2} = g_{out}$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2} = g_{out}$$

14.1) (d)

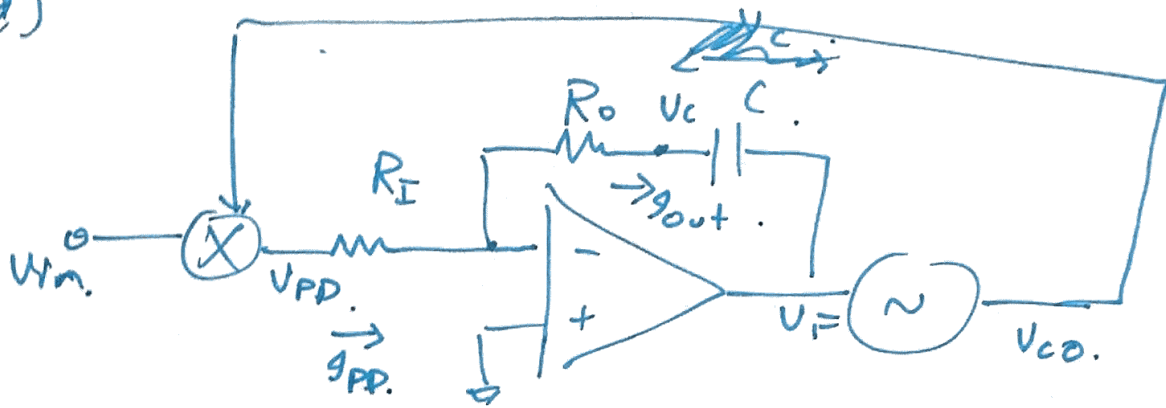

$$I_{PD} = I_{OUT}$$

$$\frac{V_{PD}}{R_I} = C \frac{dV_C}{dt}$$

$$= C \frac{d}{dt} [V_C - V_F]$$

$$\frac{V_{PD}}{R_I C} = \frac{dV_C}{dt} - \frac{dV_F}{dt}$$

$$\frac{dV_F}{dt} = \frac{dV_C}{dt} - \frac{V_{PD}}{R_I C}$$

$$\frac{dV_F}{dt} = -\frac{R_O}{R_I} \frac{dV_{PD}}{dt} - \frac{V_{PD}}{R_I C}$$

$$V_C = -I_{OUT} R_O$$

$$V_C = \frac{V_{PD}}{R_I} (-R_O)$$

$$V_C = -\frac{R_O}{R_I} V_{PD}$$

$$14.5 > \text{SNR} = 20 \log_{10} \left(\frac{V_{\text{RMS signal}}}{V_{\text{RMS noise}}} \right)$$

$$V_{\text{RMS noise}} = 1 \text{ LSB}$$

$$V_{\text{RMS signal}} = \text{Full scale signal} = 2^N \text{ LSB.}$$

$N = \text{Resolution of ADC}$

$$\text{For an 8-bit ADC } \text{SNR} = 20 \log_{10} (2^8) \\ = \underline{\underline{48.164 \text{ dB}}}$$

$$\text{For an 16-bit ADC } \text{SNR} = \underline{\underline{96.32 \text{ dB}}}$$

Averaging

$$\text{Upon averaging } (\text{SNR})_{8\text{ bit}} = 96.32 = 20 \log_{10} \left(\frac{V_{\text{RMS Avg signal}}}{V_{\text{RMS noise}}} \right)$$

$$\left(\frac{V_{\text{RMS signal}}}{V_{\text{RMS noise}}} \right)_{\text{Aver}} = 2^{16} = 2^8 \cdot 2^8 = 2^8 \left(\frac{V_{\text{RMS signal}}}{V_{\text{RMS noise}}} \right)$$



$$= \frac{V_{\text{RMS signal}}}{V_{\text{RMS noise}} / 2^8}$$

$$\text{No. of averages} = 2^8 = \underline{\underline{256}}$$

14.6 >




10

00 10 01 11 00

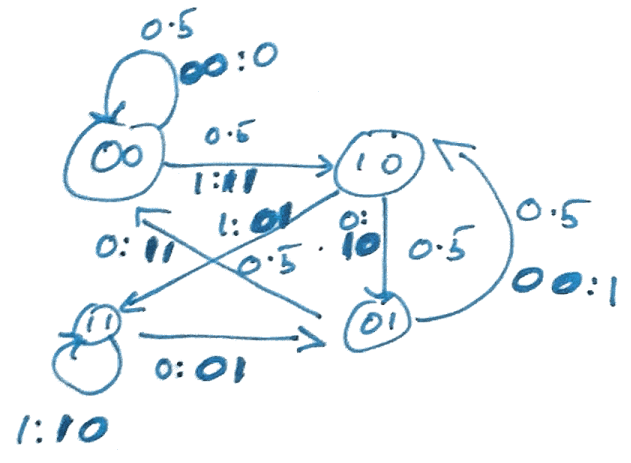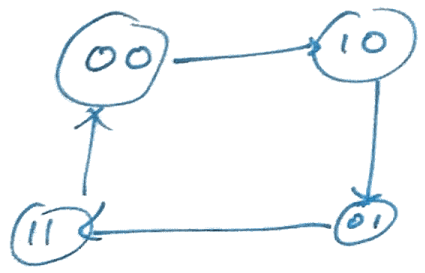

00
~~10~~

~~00 10 01 11 00~~

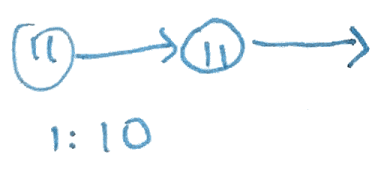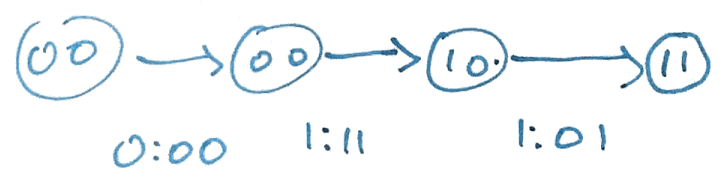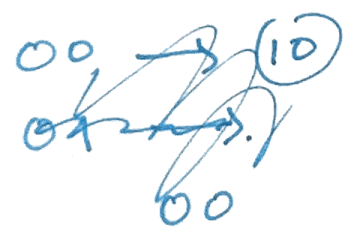


14.2) Given $\omega_1 \approx \omega_{ol} \omega_{cl} = 10 \text{ MHz}$

$$(G_{ol})_{dB} = 100 \text{ dB}$$

$$(G_{ol}) = 10^5 \cancel{\frac{R_{out}}{R_{in}}}$$

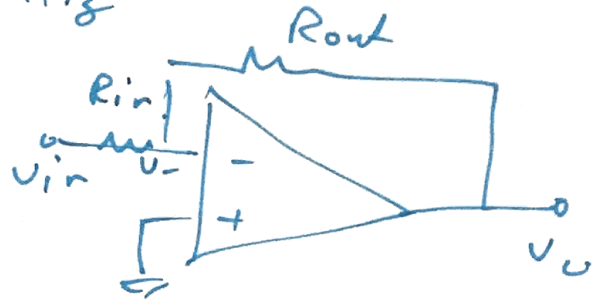~~$\omega_{ol} \approx 100 \text{ kHz}$~~



$$G(\omega) = \frac{G_{ol}}{1 + i \frac{\omega}{\omega_{ol}}}$$

$$\text{Gain with feedback} = \frac{R_{out}}{R_{in}} \cdot G(\omega) = \frac{G_{ol}}{1 + i \frac{\omega}{\omega_{ol}}}$$

~~$G(\omega) = \frac{G_{ol} \omega_{ol}}{\omega_{ol} + i \omega}$~~ ~~$= \frac{10^5}{1 + i \frac{\omega}{100 \text{ kHz}}}$~~

$$V_o = \frac{V_-}{R_{in}} G(\omega)$$

$$\frac{V_{in} - V_-}{R_{in}} = \frac{V_- - V_o}{R_{out}} \Rightarrow \frac{V_{in}}{R_{in}} + \frac{V_o}{R_{out}} = V_- \left(\frac{1}{R_{in}} + \frac{1}{R_{out}} \right)$$

$$V_- = \frac{V_{in} R_{out} + V_o R_{in}}{R_{in} R_{out}}$$

$$\therefore V_o = \left(\frac{V_{in} R_{out} + V_o R_{in}}{R_{in} + R_{out}} \right) G(\omega) \Rightarrow V_o \left(1 - \frac{R_{in}}{R_{in} + R_{out}} \right) = \frac{V_{in} R_{out}}{R_{in} + R_{out}}$$

$$V_o \left(\frac{R_{out}}{R_{in} + R_{out}} \right) = \frac{V_{in} R_{out}}{R_{in} + R_{out}}$$

$$V_o \left(1 + \frac{R_{in} G(\omega)}{R_{in} + R_{out}} \right) = \frac{-V_{in} R_{out} G(\omega)}{R_{in} + R_{out}}$$

$$V_o \left(\frac{R_{in} + R_{out} + R_{in} G(\omega)}{R_{in} + R_{out}} \right) = \frac{-V_{in} R_{out} G(\omega)}{R_{in} + R_{out}}$$

$$\frac{V_o}{V_{in}} = \frac{-R_{out} G(\omega)}{R_{in} + R_{out} + R_{in} G(\omega)}$$

$$= \frac{-\frac{R_{out}}{R_{in}} G(\omega)}{\frac{R_{out}}{R_{in}} + 1 + G(\omega)}$$

$$\frac{R_{out}}{R_{in}} + 1 + G(\omega)$$




$$= \frac{-\frac{R_{out}}{R_{in}} \frac{G_{ol}}{1 + i\omega/\omega_{ol}}}{1 + \frac{R_{out}}{R_{in}} + \frac{G_{ol}}{1 + i\omega/\omega_{ol}}}$$

$$1 + \frac{G_{ol}}{1 + i\omega/\omega_{ol}} + \frac{R_{out}}{R_{in}}$$

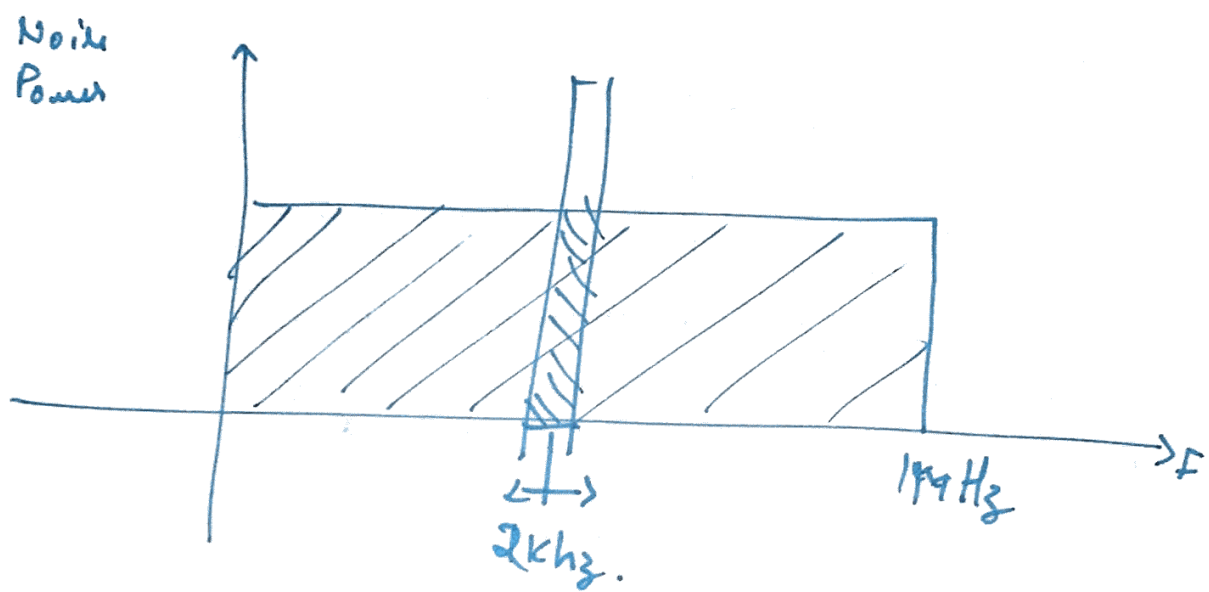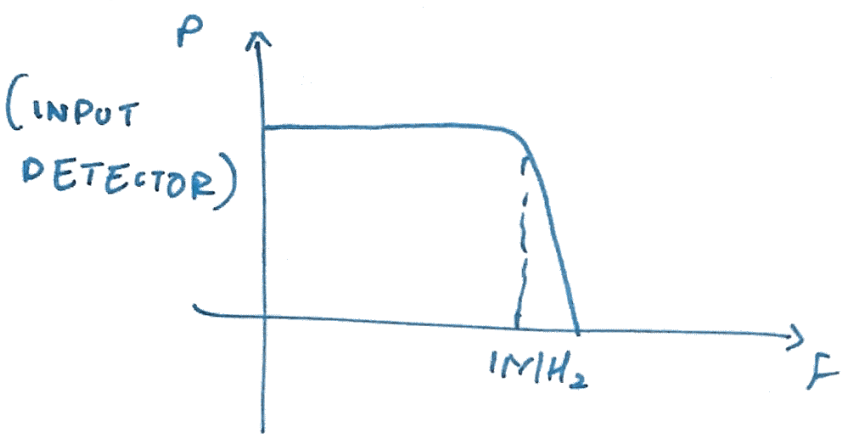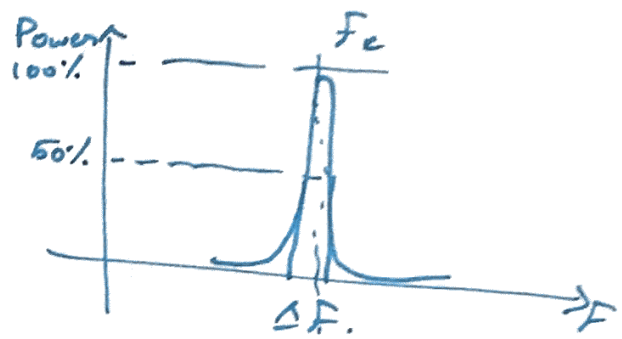14.3

$$f_0 = 100 \text{ kHz}, \quad Q = 50 = \frac{f_c}{\Delta f}$$

$$\Delta f = \frac{100 \text{ kHz}}{50} = 2 \text{ kHz}.$$



Reduction factor. = $\frac{1 \text{ MHz}}{2 \text{ kHz}} = 500$
 at bandpass filter.