

11.2) We have expected occupancy =  $\frac{1}{1 + e^{\left(\frac{E - E_F}{kT}\right)}}$

$$= \frac{1}{1 + e^{\left(\frac{E_F + E_g}{(2 - E_F)kT}\right)}} = \frac{1}{1 + e^{\frac{E_g}{2kT}}}$$

For Germanium =  $\frac{1}{1 + e^{\frac{0.67 \text{ eV}}{2kT}}}$

$$kT = 8.617 \times 10^{-5} \times 300 = 0.026 \text{ eV}$$

For Germanium =  $2.5 \times 10^{-6}$

For Silicon =  $5.4 \times 10^{-10}$


For diamond =  $1.7 \times 10^{-42}$

$$11.5) a) \text{ Energy in capacitor} = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \times 10 \times 10^{-15} \times 5^2$$

$$= 1.25 \times 10^{-13} \text{ J}$$

b)

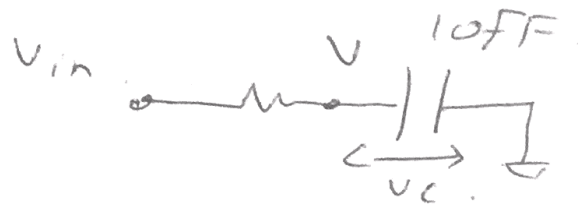

$$I = \frac{V_{in} - V}{R} = C \frac{dV_C}{dt}$$

$$\frac{dV_C}{dt} = \frac{1}{RC} (V_{in} - V), \quad V = V_C$$

$$V_C = V (1 - e^{-t/RC})$$

$$I = \frac{V}{R} e^{-t/RC}$$

$$\text{Power dissipated} = \int_0^{\infty} \frac{V^2}{R} dt = \int_0^{\infty} I^2 R dt$$

$$= \int_0^{\infty} \frac{V^2}{R^2} e^{-2t/RC} \cdot R dt = \frac{V^2}{R} \int_0^{\infty} e^{-\frac{2t}{RC}} dt$$

$$= \frac{V^2}{R} \left( \frac{1}{-2} \right) e^{-2t/RC} \Big|_0^{\infty} = \frac{2V^2}{R^2 C} = \frac{1}{2} C V^2$$

We have  $\frac{dV_c}{dt} = \frac{1}{RC} (V_{in} - V_c)$

(d) Energy stored in charging =  $\frac{1}{2} CV^2$

Energy dissipated in discharging =  $\frac{1}{2} CV^2$

Total energy =  $CV^2 = 10 \times 10^{-15} \times 5^2 = 2.5 \times 10^{-13} \text{ J}$

Power =  $1 \text{ W}$

~~Fr~~  $\therefore$  Frequency at which

charge and discharge happens =  $\frac{1}{2.5 \times 10^{-13}} =$

$= 40 \times 10^{11} \text{ Hz}$

$= 4 \times 10^{12} \text{ Hz}$

e)  $2.5 \times 10^{13} \text{ J (per transition)}$   
     $\times$   
     $10^6 \text{ Transition.}$   
     $\times$   
     $100 \times 10^6$  } =  $25 \text{ W}$

F) Charge in a capacitor  $Q = 10$ .

$$= 10 \times 10^{-15} \times 5 = 5 \times 10^{-14} \text{ C.}$$

$$\text{No. of electrons} = \frac{5 \times 10^{-14}}{1.6 \times 10^{-19}} = \underline{\underline{3 \times 10^5 \text{ electrons}}}$$