

FabLab presentation

Power Electronics in Electrical Motors Controls

Xu Sun


Motor Types

- **AC motor**
driven by single-phase or three-phase commercial AC
- **DC motor**
driven by DC (batteries or AC/DC converters)
- **Precision motor**
electronically controlled stepping motors (hybrid or variable-reluctance or permanent-magnet)

Comparison of Motors


- AC/DC motors ---- analog rotation
- Stepping motors ---- digital rotation
 1. Hybrid: small step length, high torque, position preserved during power failure
 2. Variable-reluctance: longer revolution (due to large step), faster acceleration (low inertial load due to no permanent-magnet in rotor)

Motor Control

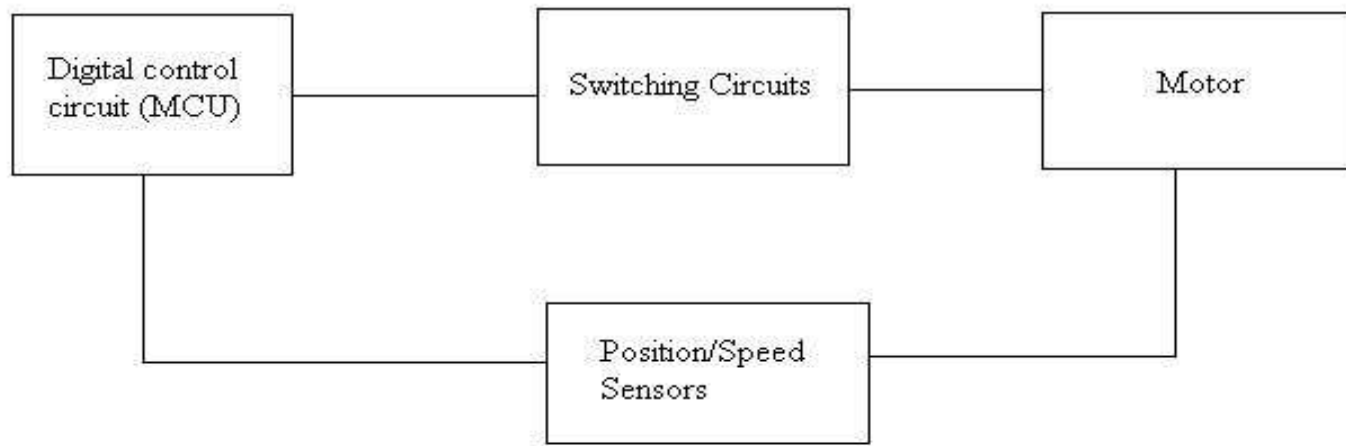


Switching Circuits

I. Unipolar motor control

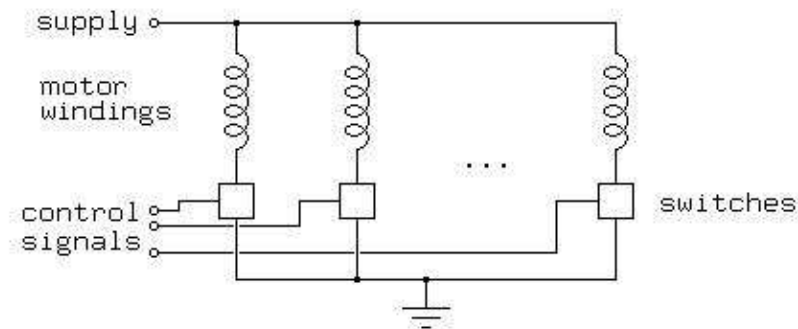


**Unipolar DC
VR stepping**

General control block

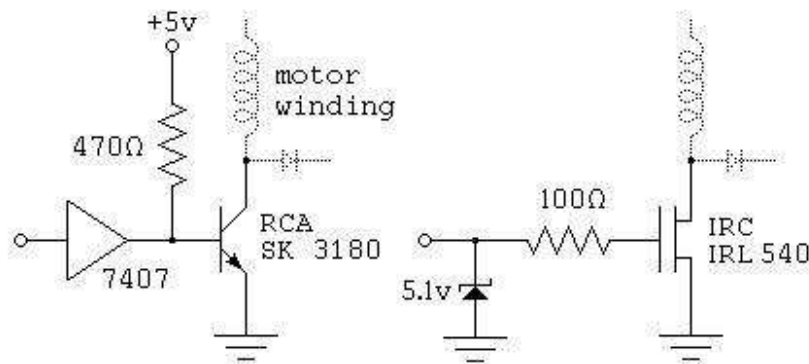


Switching circuits

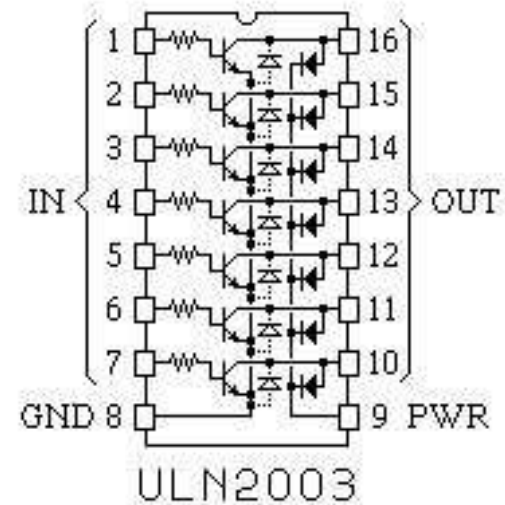


Commercial chips

Switching Circuits


II. Bipolar motor control

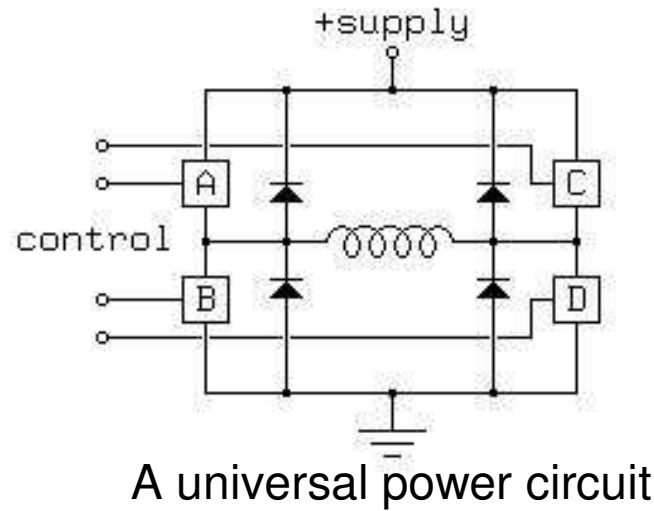

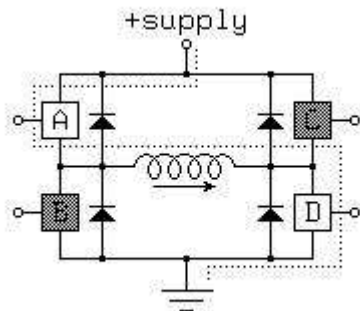
**Bipolar DC
Permanent-magnet
Hybrid Stepping**



XY ABCD Mode
01 1001 **forward**

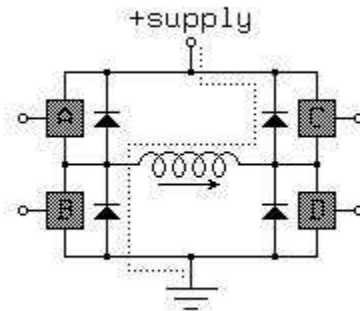


XY ABCD Mode
00 0000 **fast decay**

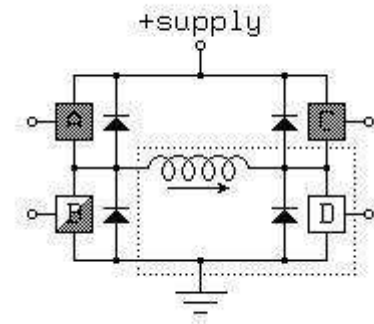

XY ABCD Mode
11 0101 **slow decay**


Switching Circuits

II. Bipolar motor control

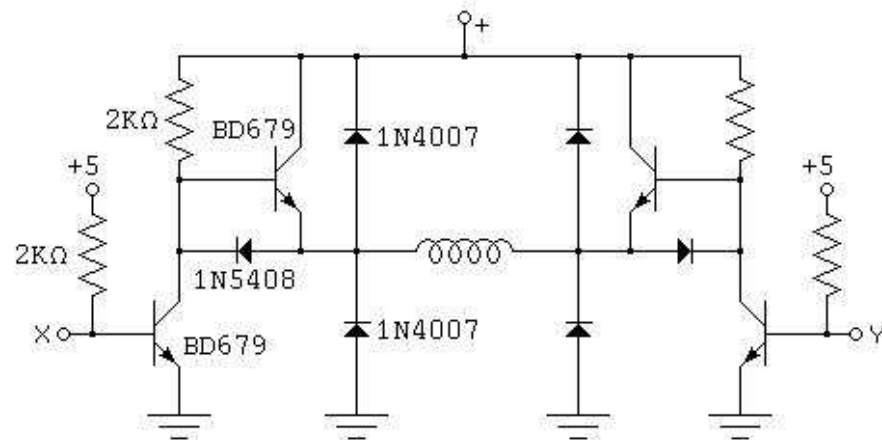


74LS125A/ 74LS244
 TC4467 18V/250mA
 L293 36V/1A
 LMD18200 3A
 IR2104 high V, I
 TC4467 CMOS

A practical bipolar switching circuit

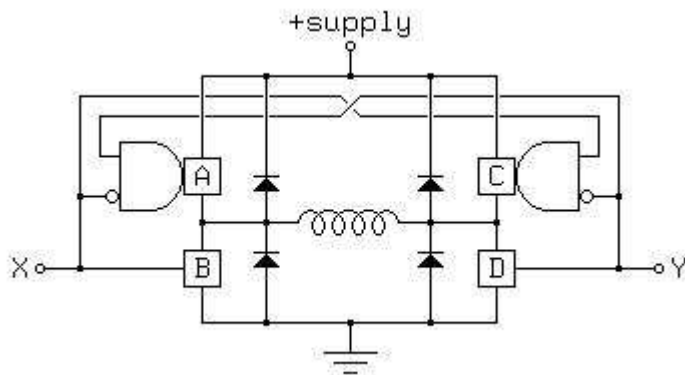

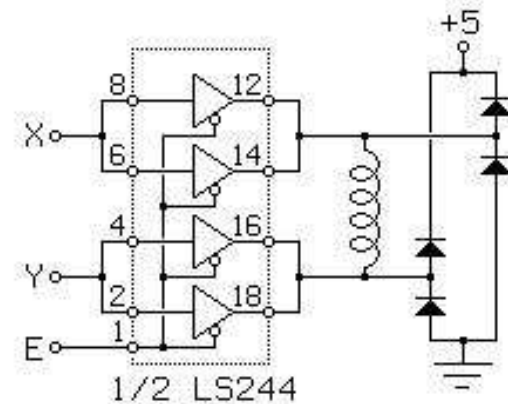A simple circuit with digital coding gate





Commercial chips

Device Selection

- **BJT**
require high base drive power
- **Darlington**
high current gain
- **MOSFET**
negligible drive power
- **IGBT**
high voltage high current case

Digital Control

Open loop or close loop?

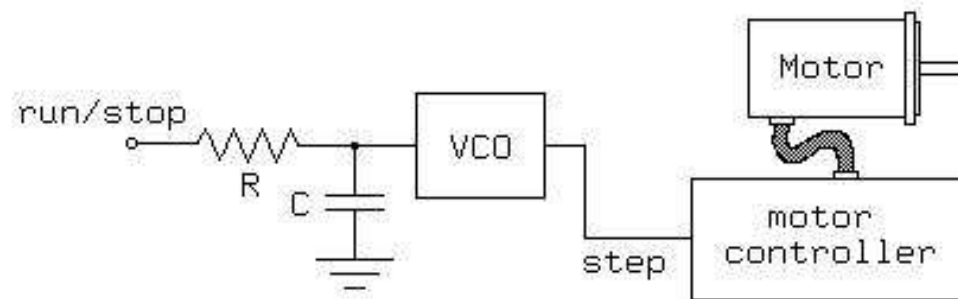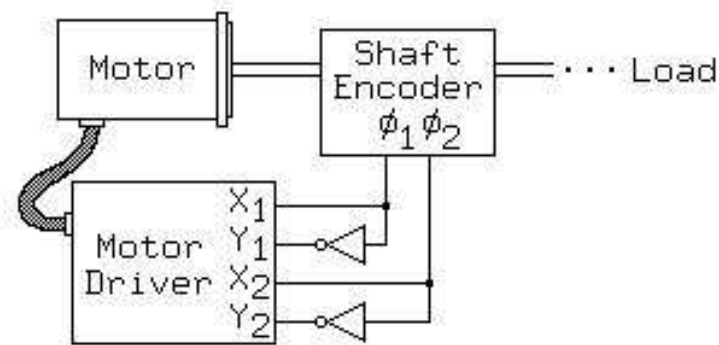

Reference

- Control of Stepping Motors
<http://www.cs.uiowa.edu/~jones/step/>
- Electric Motors and their Controls
by Tak Kenjo, Oxford Science Publications
- Stepping Motors a guide to theory and practice
by Paul Acarnley, 4th edition, IEE
- Foundations of Electric Power
by J.R.Cogdell, Prentice Hall