


18.1) a)

(ideal) op amps: current into inputs is 0

$$V_{out} = G \cdot \text{input}$$

inputs are kept the same

Integrator

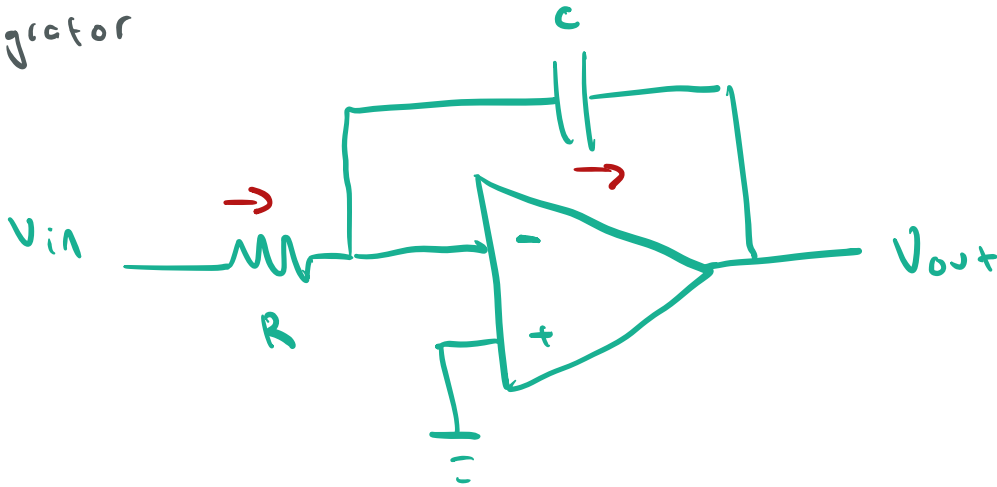

Using KCC (Kirchhoff's current law)

current through R:

$$V = IR$$

$$I = \frac{V_{in}}{R}$$

current through cap

$$I = C \frac{dV_o}{dt}$$


R & C
are
constants

$$\frac{V_{in}}{R} = C \frac{dV_o}{dt}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

Differentiator

Swap $R \leftrightarrow C$

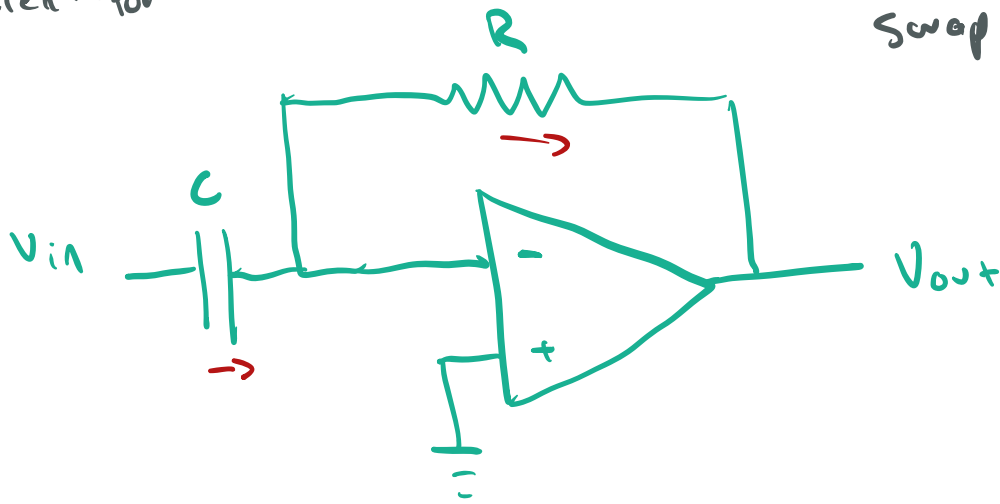

- otherwise opposite direction


now :

$$C \frac{dV_i}{dt} = -\frac{V_o}{R}$$

$$V_o = -RC \frac{dV_i}{dt}$$

SUMMING

(assuming all R_{in} s are the same)

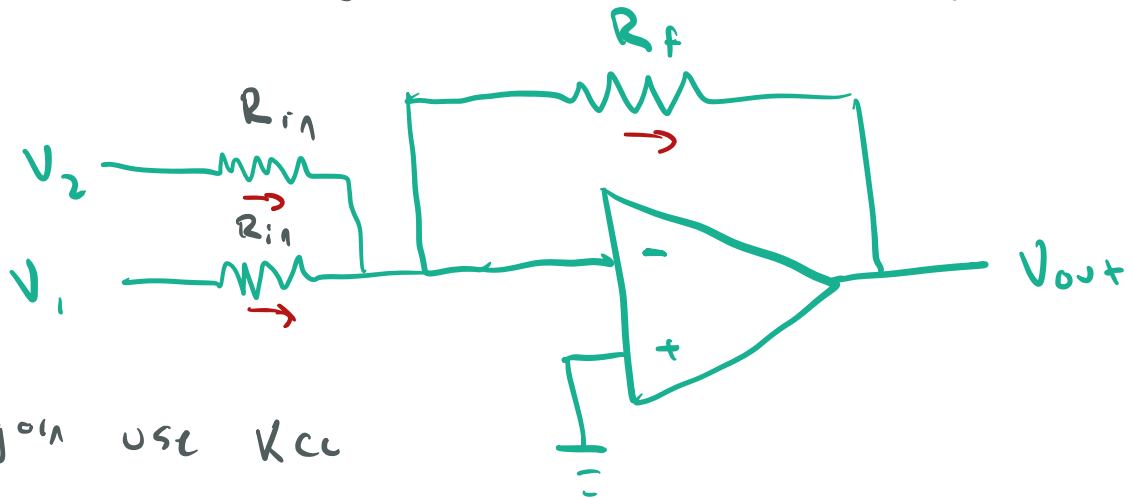


again use KCL

$$\frac{\sum V_{in}}{R_{in}} = -\frac{V_o}{R_f}$$

$$V_o = -\frac{\sum V_{in}}{R_{in}} (R_f)$$

Differential Amp

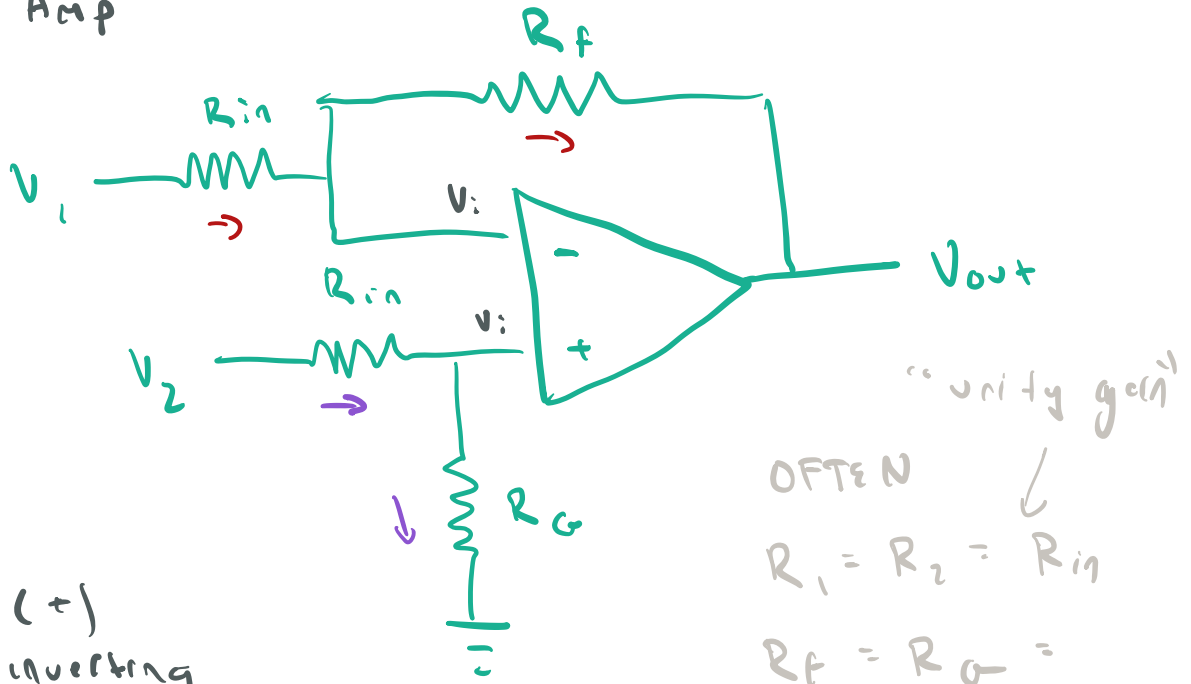

(+)
KCC to non-inverting

$$\frac{V_2 - V_{in}}{R_{in}} = \frac{V_{in}}{R_G}$$

$$\frac{V_2}{R_{in}} = \frac{V_{in}}{R_G} + \frac{V_{in}}{R_{in}}$$

(-)
KCC to inverting

$$\frac{V_1 - V_{in}}{R_{in}} = \frac{V_{in} - V_o}{R_F}$$


write it
all out

$$\frac{V_1}{R_{in}} - \frac{V_{in}}{R_{in}} = \frac{V_{in}}{R_F} - \frac{V_o}{R_F}$$

$$\frac{V_1}{R_{in}} + \frac{V_o}{R_F} = V_{in} \left(\frac{1}{R_{in}} + \frac{1}{R_F} \right) = \frac{V_2}{R_{in}}$$

$$V_o = \frac{V_2}{R_{in}} - \frac{V_1}{R_{in}} (R_F) \quad \therefore V_o = \frac{R_F}{R_{in}} (V_2 - V_1)$$

15.1) b)

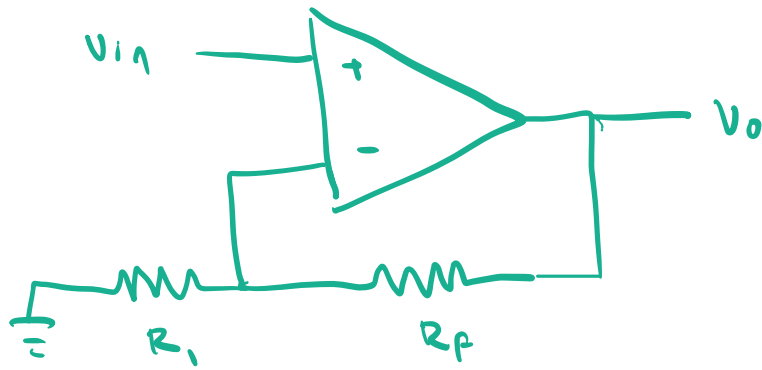

KCC:

$$\frac{V_o - V_{in}}{R_f} = \frac{V_{in}}{R_i}$$

$$V_o = \frac{R_f}{R_i} V_{in} + V_{in}$$

$$= V_{in} \left(\frac{R_f}{R_i} + 1 \right)$$

one downside is that we can only amplify up


because of the $+1$ (an inverting amp is $= -V_{in} \frac{R_f}{R_i}$)

Also we have R_i between Gnd & our inverting input so poorer common mode noise rejection

15.1) c)

Transimpedance

V_{out} proportional to I_{in}

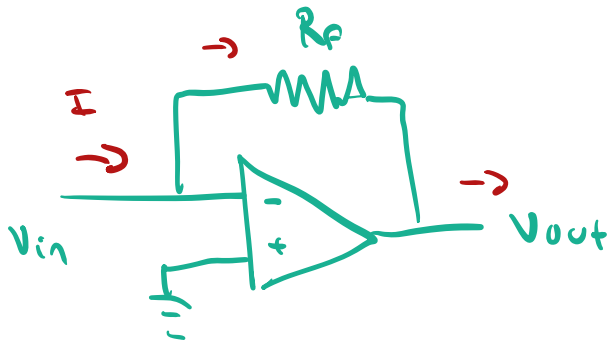


KCC

$$I = \frac{V_o}{R_f}$$

so proportional to R_f

Transconductance

I_{out} proportional to V_{in}

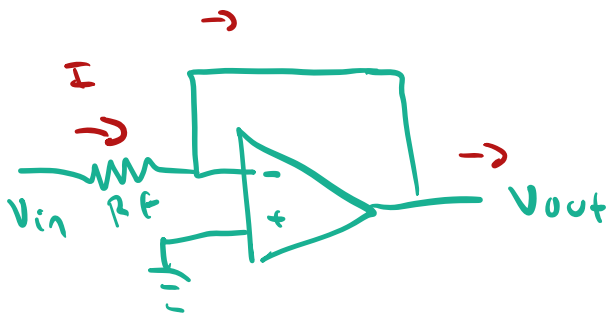

$$I_{out} = \frac{V_{in}}{R_f}$$


15.1) d)

Lock in amps amplify weak & repetitive signals buried in noise

Input 1 = noisy signal

Input 2 = reference signal with same frequency as desired signal

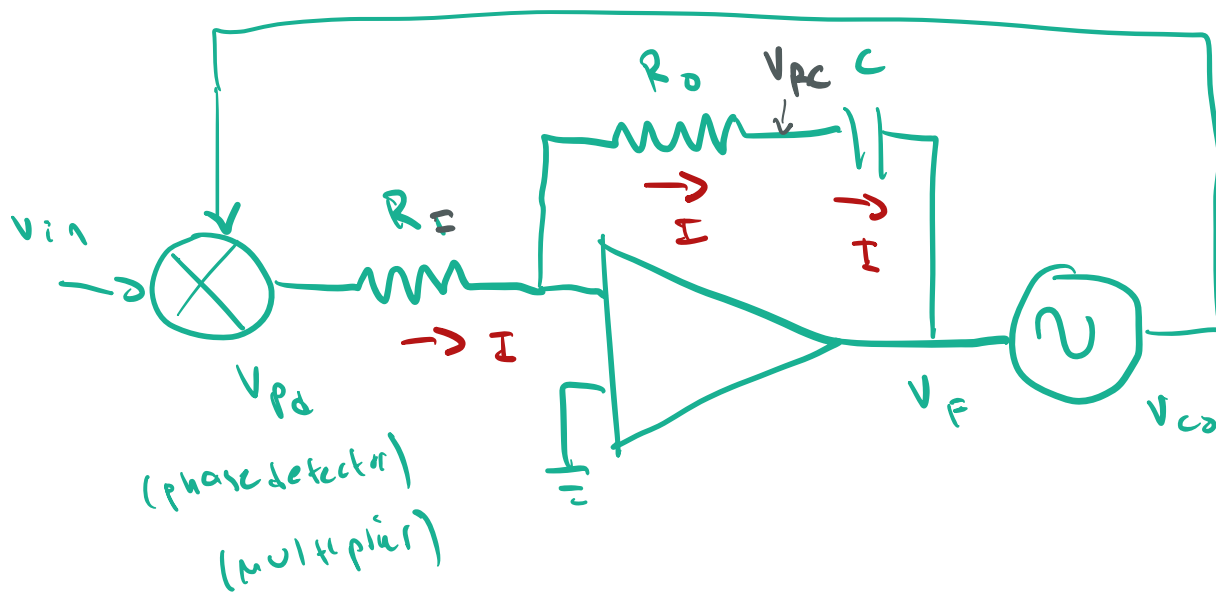Output represents amplitude of desired signal & phase relationship to reference.



we are given

$$\frac{dV_F}{dt} = - \frac{R_O}{R_I} \cdot \frac{dV_{Pd}}{dt} - \frac{V_{Pd}}{R_I C}$$

Using KCL :

$$I R_E = I_{R_0} = I_C$$

for a cap
 $I = C \frac{dV}{dt}$

(1)

$$I = \frac{V_{pd}}{R_I}$$

- or - (2)

$$I = \frac{-V_{Rc}}{R_0}$$

- or - (3)

$$I = C \left(\frac{dV_{Rc}}{dt} - \frac{dV_F}{dt} \right)$$

↓ differentiate

↓

$$\frac{dI}{dt} = \frac{dV_{pd}}{dt R_I}$$

$$\frac{dI}{dt} = - \frac{dV_{Rc}}{dt R_0}$$

plug these
into (3)

$$\frac{dV_{Rc}}{dt} = - \frac{dV_{pd}}{dt} \cdot \frac{R_0}{R_I}$$

$$\text{so: } I = C \left(- \frac{dV_{pd}}{dt} \cdot \frac{R_0}{R_I} - \frac{dV_F}{dt} \right) = \frac{V_{pd}}{R_I}$$

now we solve for $\frac{dV_F}{dt}$

$$\frac{dV_F}{dt} = - \frac{V_{pd}}{R_I \cdot C} - \frac{dV_{pd}}{dt} \cdot \frac{R_0}{R_I}$$

(sign is just convention)