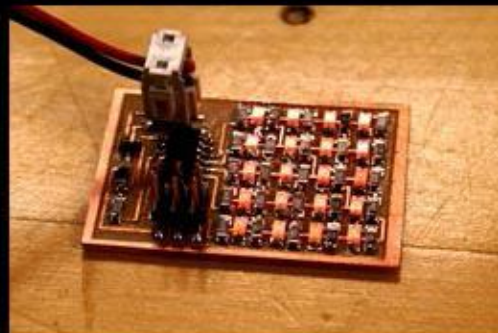


MAS 863  
*How To Make (almost) Anything*  
2009

Output Devices




LCD - 44780



LED Array - Charlieplexing



DC Motor - H-Bridge

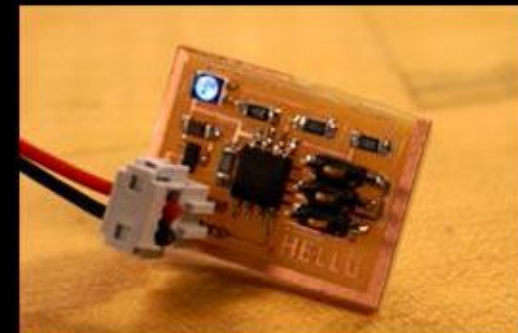

RGB LED - PWM



Video - RS170










Stepper Motor




Speaker - MOSFET

# LED Array Charlieplexing

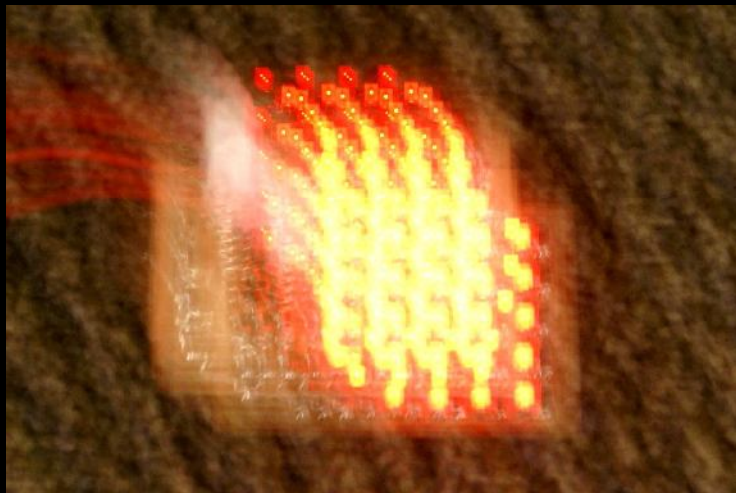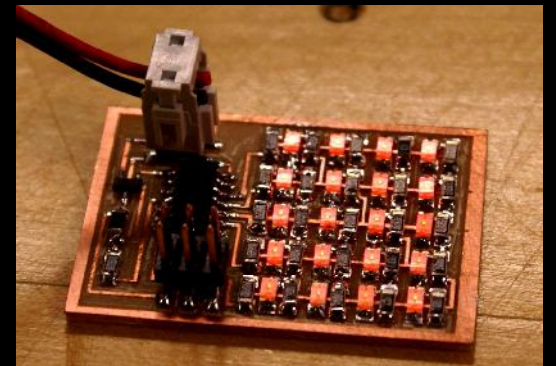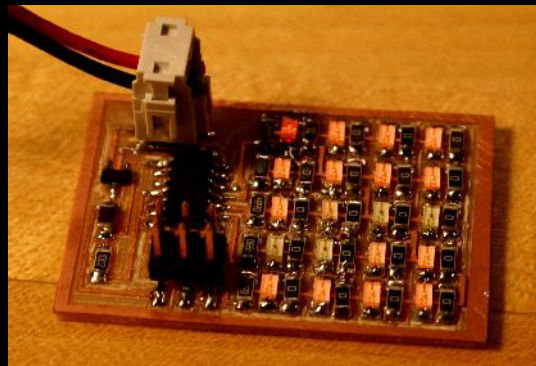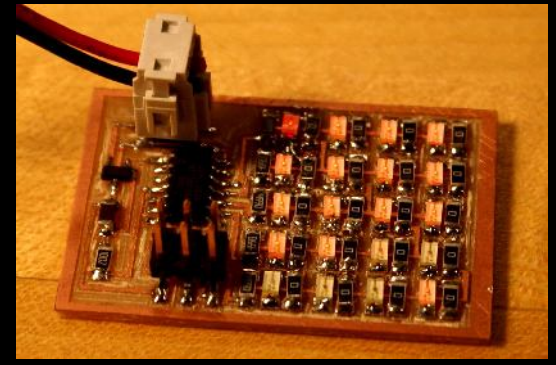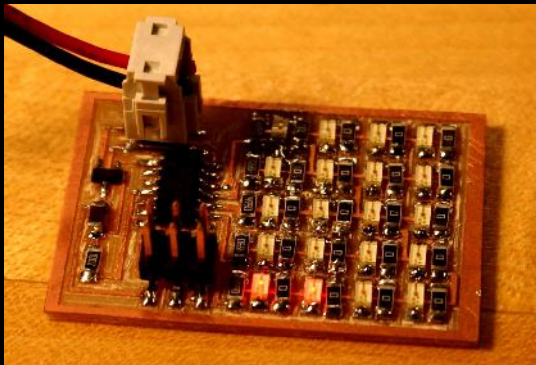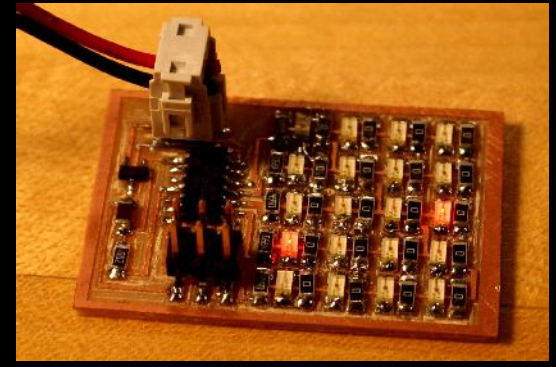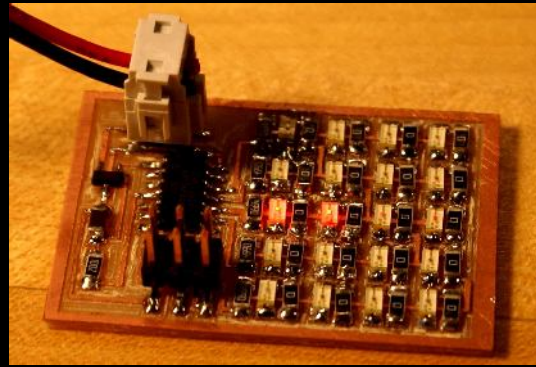




## RGBLED

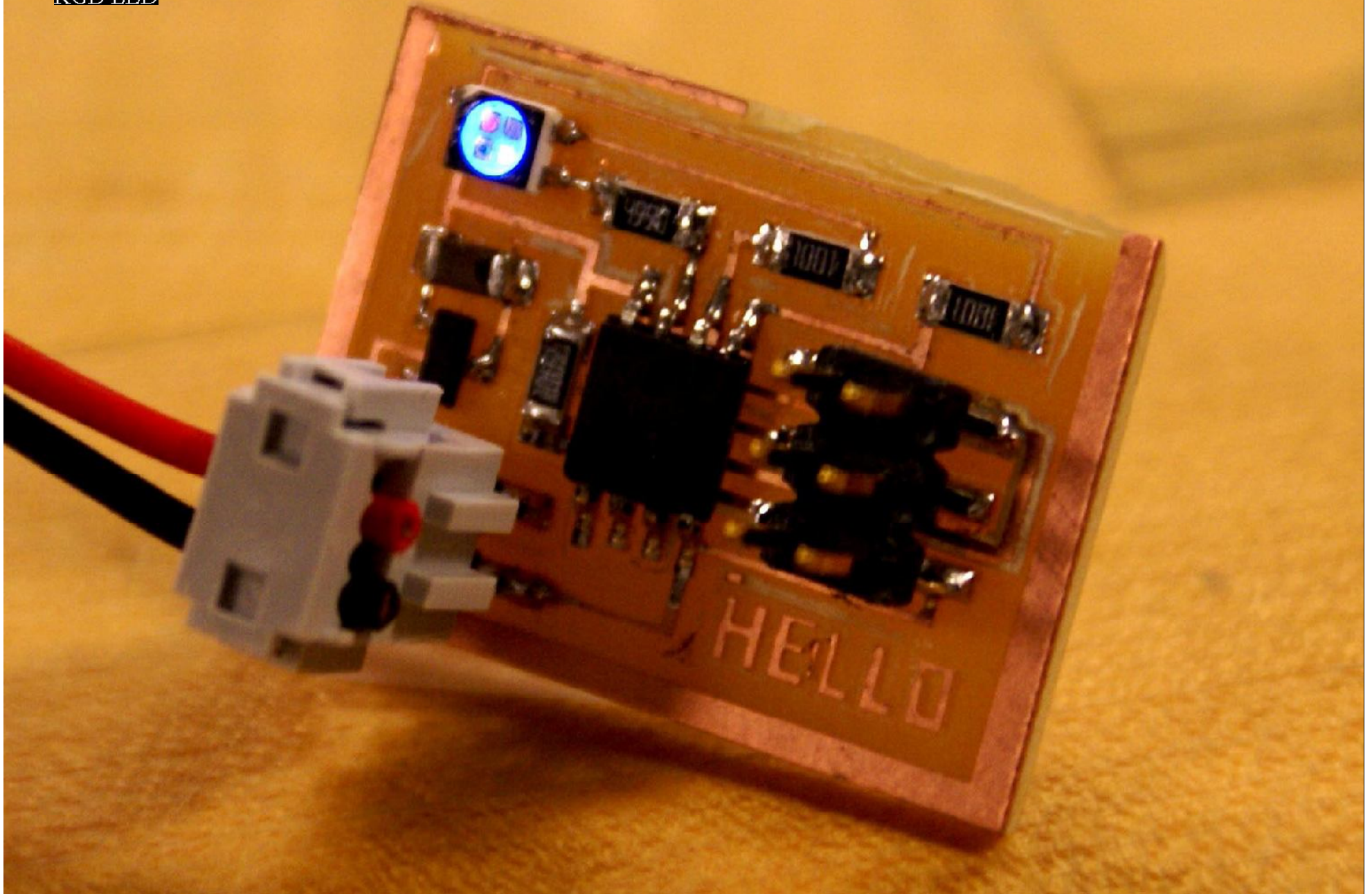




## DC Motor – H-Bridge




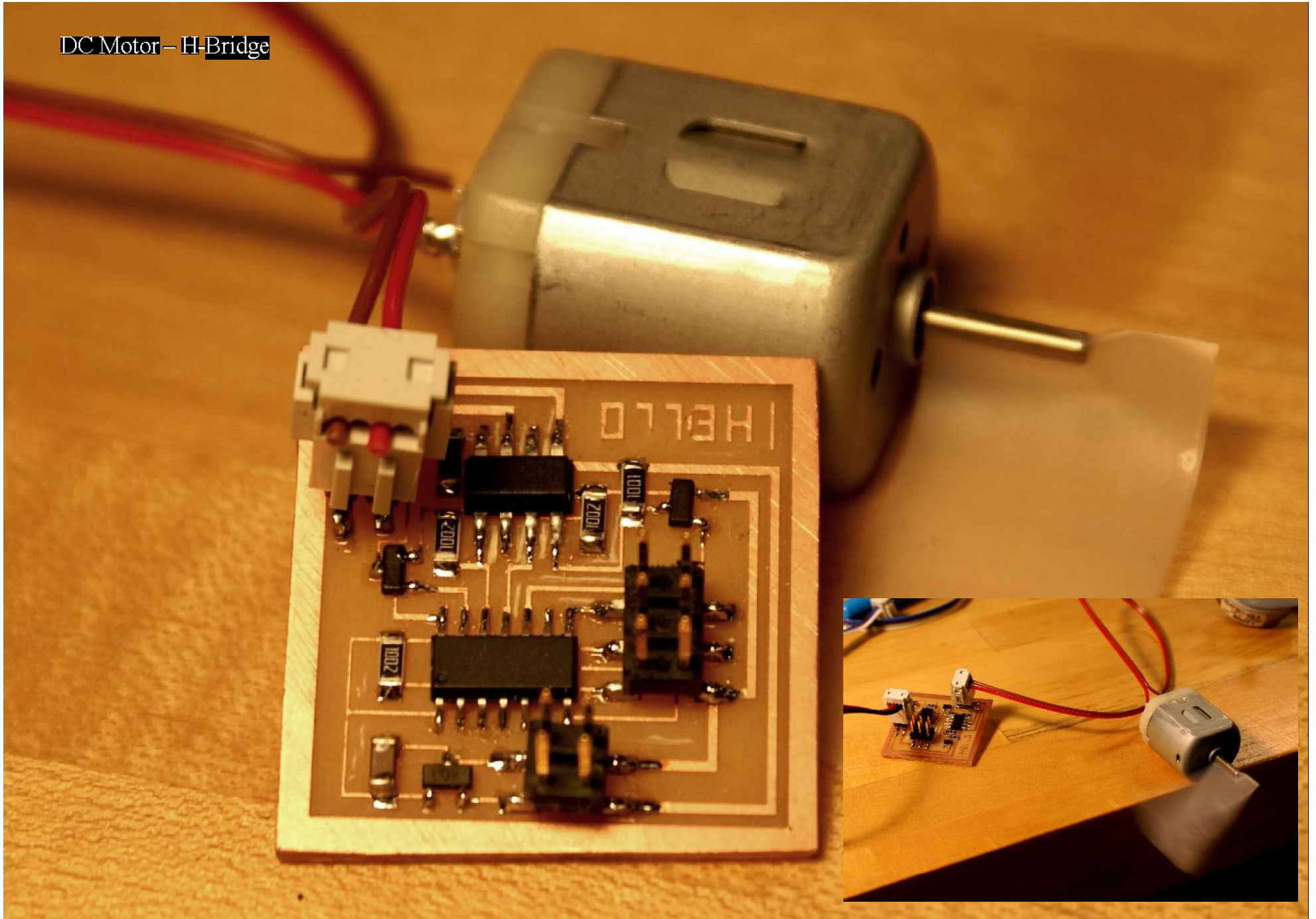





Speaker - MOSFET

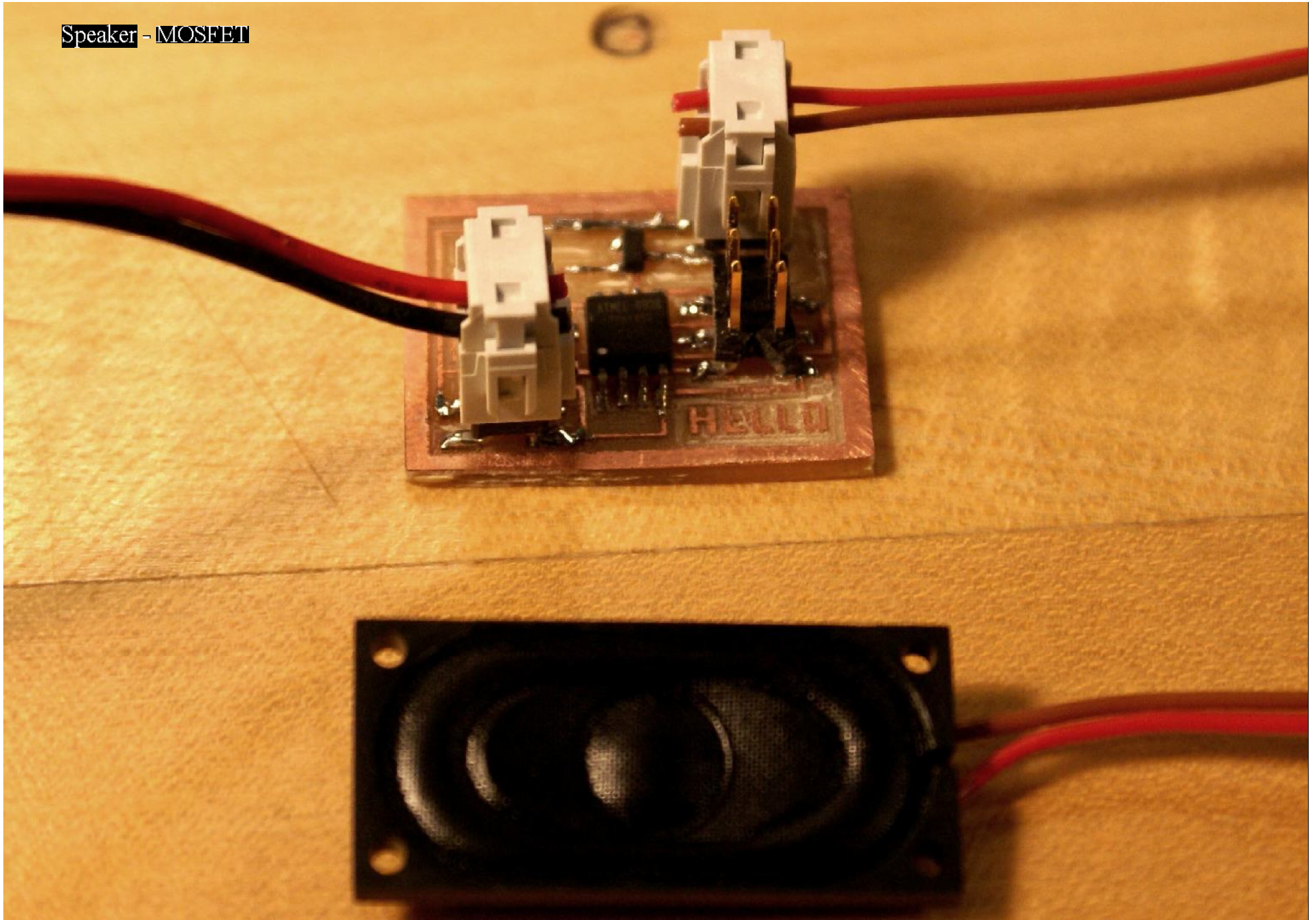

## Stepper Motor

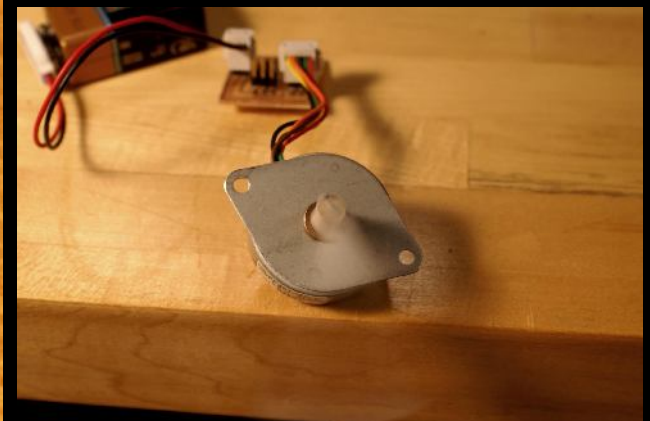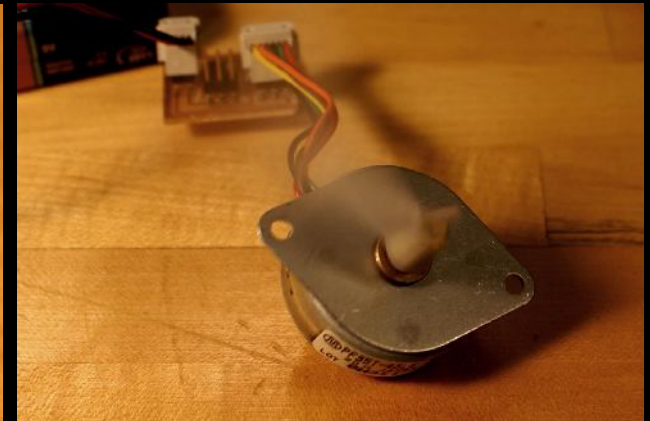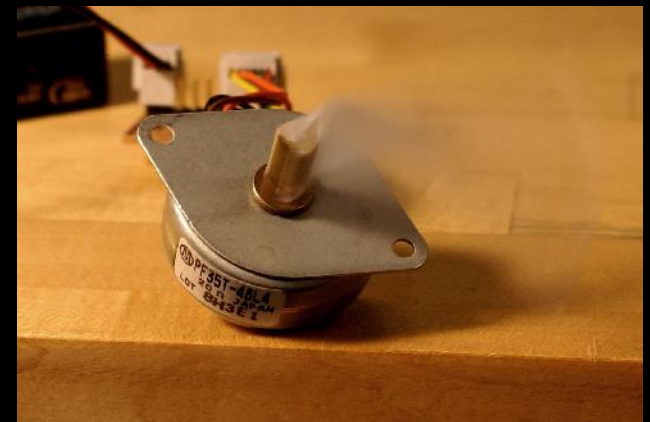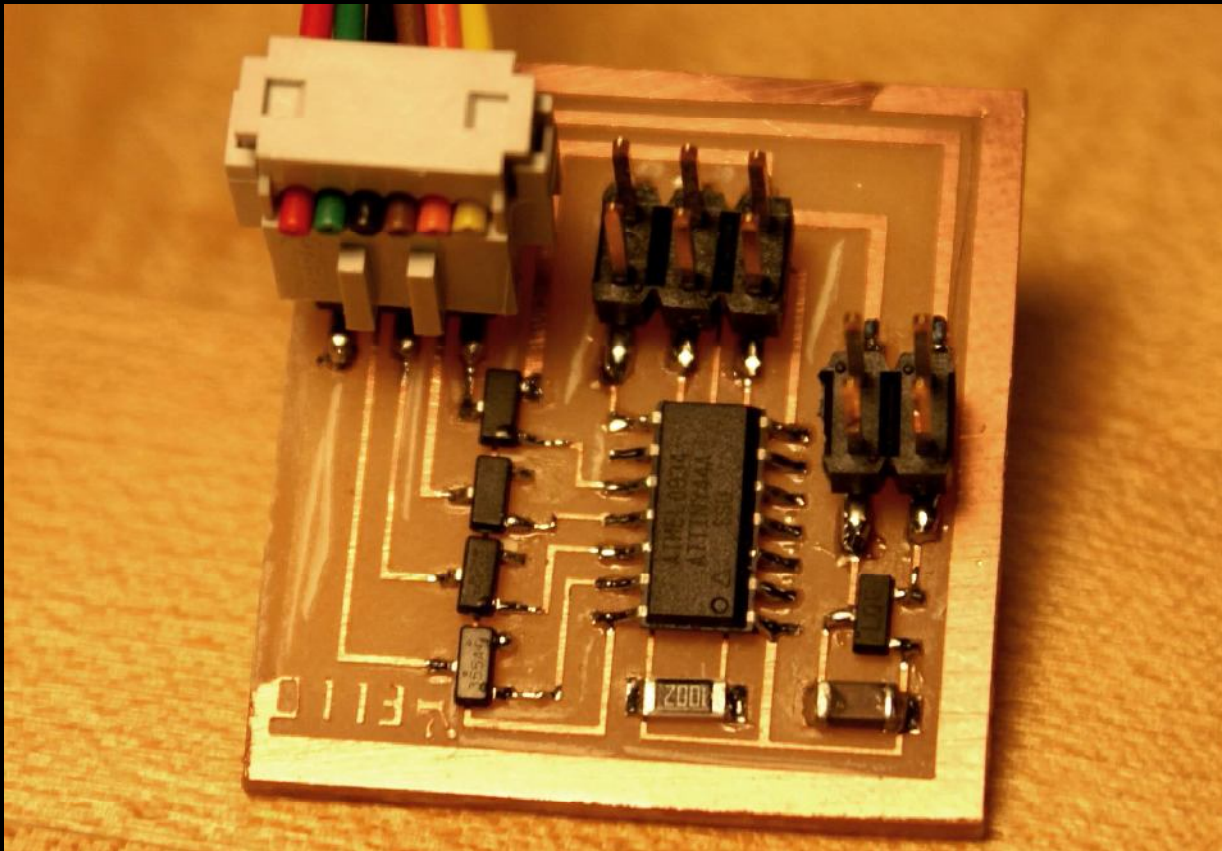



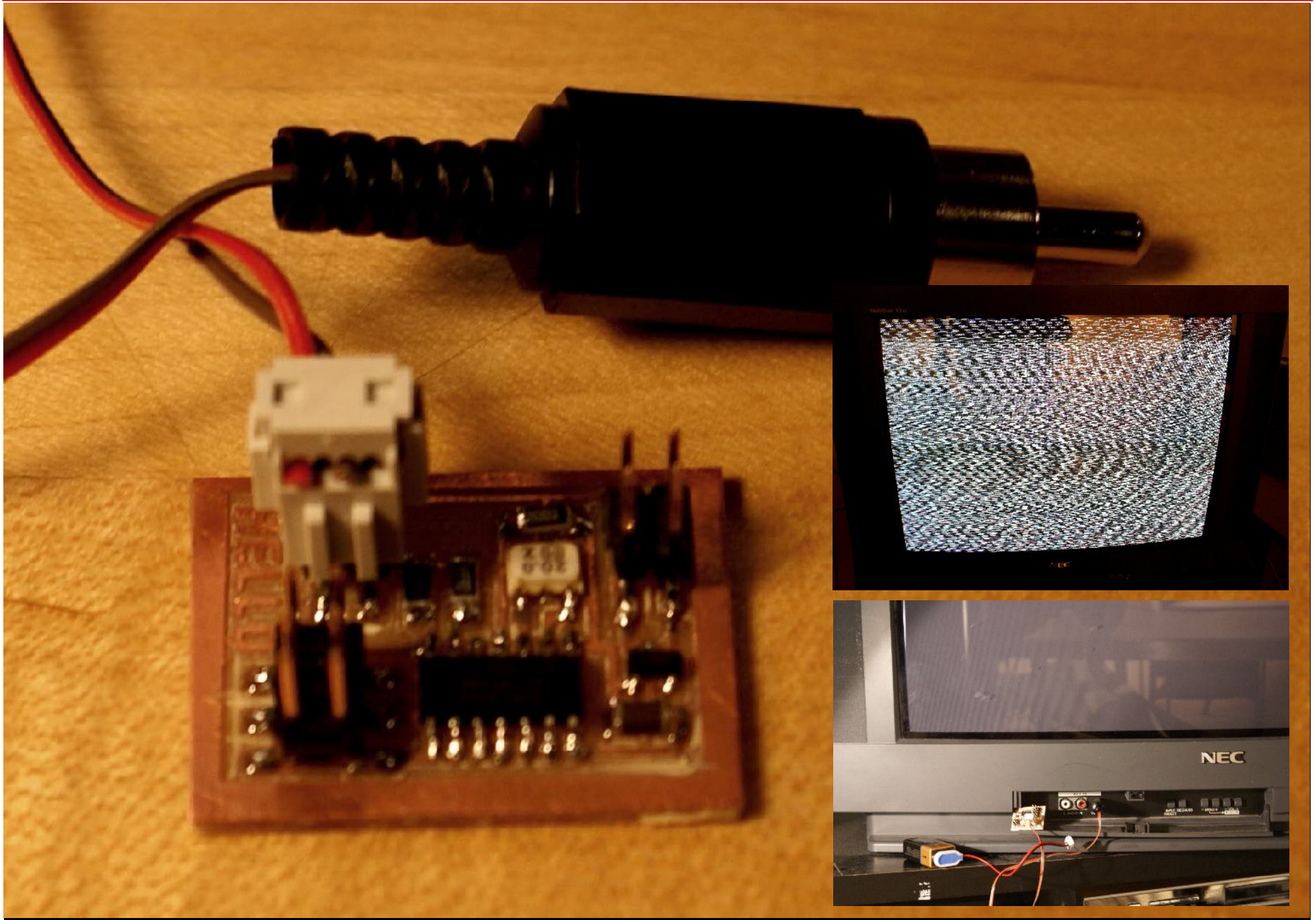



LCD - 44780

